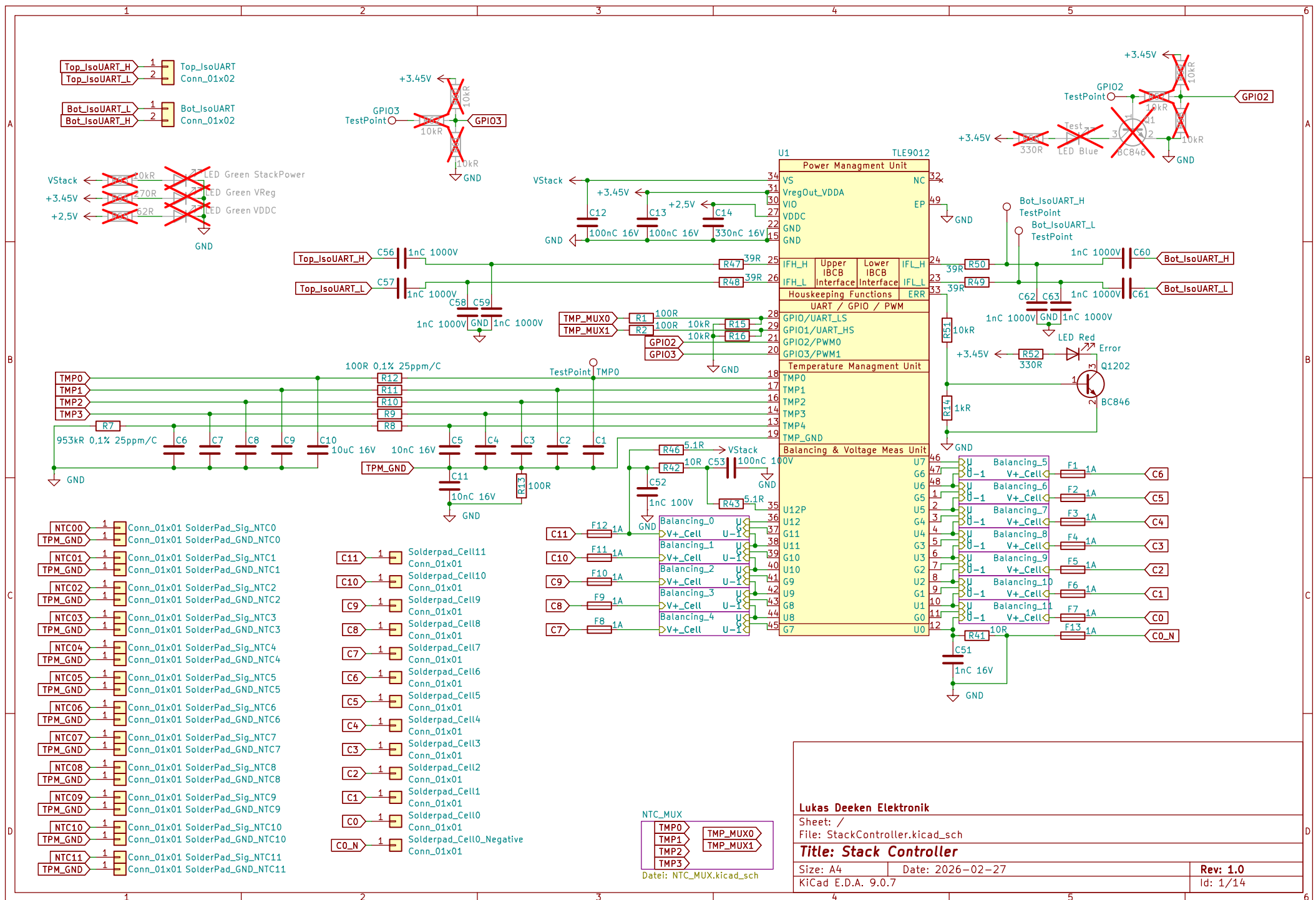






R gegen GND ist zur
Diagnose für 10k NTC
B3950 TNom25°C
866k = -49,96°C
887k = -50,26°C
909k = -50,57°C
931k = -50,87°C
953k = -51,16°C



Id: 2/14


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

R_F = 100hm
R_{Switch_min} = 1.60hm
R_{Bal} = 390hm

U_{Max_cell} = 4,25V

I_{Max_bal} = 4,25V/29,60hm =
143,6mA

halbieren paralleler
stromfluss?

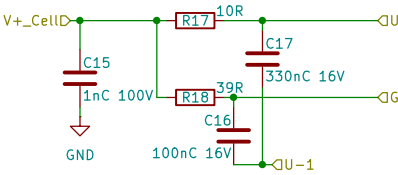

Lukas Deeken Elektronik

Sheet: /Balancing_0/
File: Balancing.kicad_sch

Title: Stack Controller

Size: A4

Date: 2026-02-27

Rev: 1.0

KiCad E.D.A. 9.0.7

Id: 3/14


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

R_F = 100hm
R_{Switch_min} = 1.60hm
R_{Bal} = 390hm

U_{Max_cell} = 4,25V

I_{Max_bal} = 4,25V/29,60hm =
143,6mA

halbieren paralleler
stromfluss?

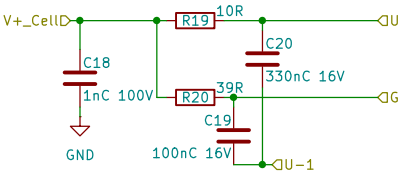


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

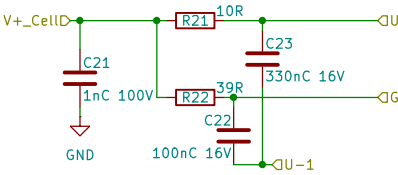


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

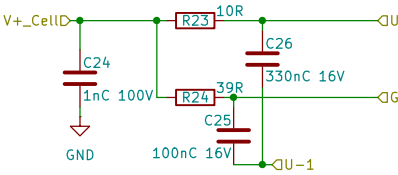

Lukas Deeken Elektronik

Sheet: /Balancing_3/
File: Balancing.kicad_sch

Title: Stack Controller

Size: A4

Date: 2026-02-27

Rev: 1.0

KiCad E.D.A. 9.0.7


Id: 6/14

Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

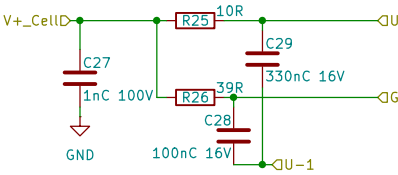


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

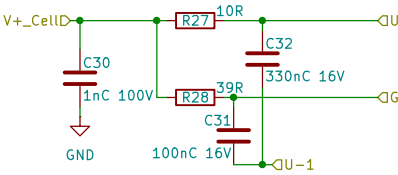


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

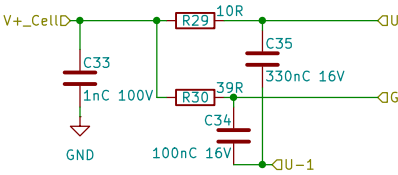


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

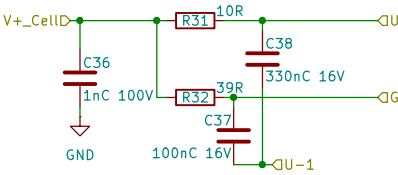

Lukas Deeken Elektronik

Sheet: /Balancing_7/
File: Balancing.kicad_sch

Title: Stack Controller

Size: A4

Date: 2026-02-27

Rev: 1.0

KiCad E.D.A. 9.0.7

Id: 10/14


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

R_F = 100hm
R_{Switch_min} = 1.60hm
R_{Bal} = 390hm

U_{Max_cell} = 4,25V

I_{Max_bal} = 4,25V/29,60hm =
143,6mA

halbieren paralleler
stromfluss?

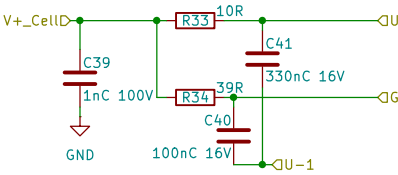

Lukas Deeken Elektronik

Sheet: /Balancing_8/
File: Balancing.kicad_sch

Title: Stack Controller

Size: A4

Date: 2026-02-27

Rev: 1.0

KiCad E.D.A. 9.0.7


Id: 11/14

Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

$R_F = 100\Omega$
 $R_{Switch_min} = 1.60\Omega$
 $R_{bal} = 390\Omega$

$U_{Max_cell} = 4,25V$
 $I_{Max_bal} = 4,25V/29,60\Omega = 143,6mA$

halbieren paralleler
stromfluss?

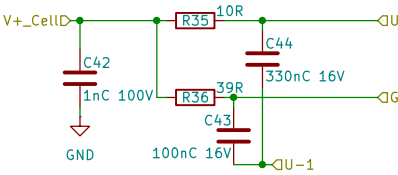

Lukas Deeken Elektronik

Sheet: /Balancing_9/
File: Balancing.kicad_sch

Title: Stack Controller

Size: A4

Date: 2026-02-27

Rev: 1.0

KiCad E.D.A. 9.0.7

Id: 12/14


Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

R_F = 100hm
R_{Switch_min} = 1.60hm
R_{Bal} = 390hm

U_{Max_cell} = 4,25V

I_{Max_bal} = 4,25V/29,60hm =
143,6mA

halbieren paralleler
stromfluss?

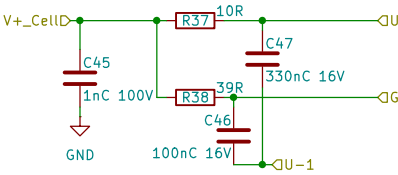

Balancing strom geht durch
R_{Bal} -> R_{Switch} -> R_F

R_F = 100hm
R_{Switch_min} = 1.60hm
R_{Bal} = 390hm

U_{Max_cell} = 4,25V

I_{Max_bal} = 4,25V/29,60hm =
143,6mA

halbieren paralleler
stromfluss?

